SIMPLE POCKET LIGHT




IDEA: Making a simple DOIT pocket light with LED.

NEEDS:

- IFD
- lithium button cell battery
- copper strip (20 cm)
- Wood stalk
- Adhesive film
- Paper clip (unpainted)
- Other materials for decoration as wishes



HOW−TO: • Construction Plan

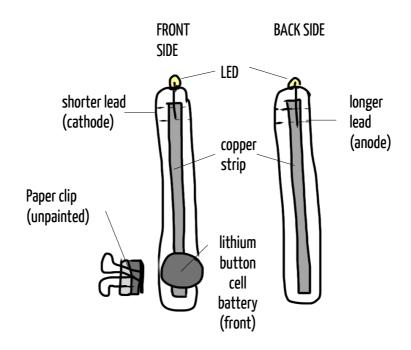

Idea is taken from Juliane Jammer & Kristin Narr: Das Maker-Buch für Kita und Grundschule (English translation included!)

